


Inclass 3/22 – Circuit Practice Problems

From Fishbane, Gasiorowicz, and Thornton


27.3. (I) A battery with an emf of 3.00 V sends a current of 1.99 A when it is connected in series with a 1.50- Ω resistor. What is the internal resistance of the battery?

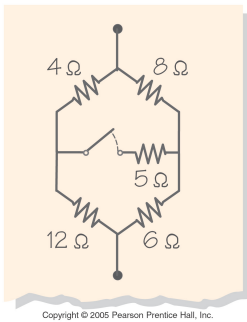27.17. (II) Consider the part of a circuit shown in Fig. 27–28. What is the total resistance if (a) the switch is open, and (b) the switch is closed?


Hint: Even though there's no battery drawn, you can imagine one battery with potential difference, V , across the entire thing. Use that in two voltage loops to simplify the algebra a bit.



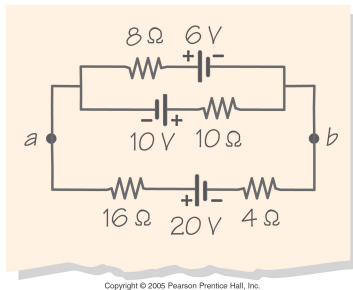27.18. (II) Consider the circuit in Fig. 27–29. Calculate the current through the 16 Ω resistor, and the voltage across ab .




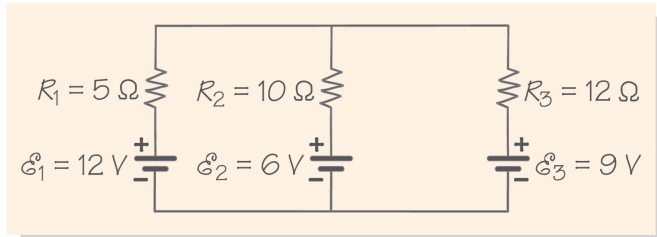27.19. (II) Find the current that passes through each of the resistors in the circuit shown in Fig. 27–30.



Copyright © 2005 Pearson Prentice Hall, Inc.

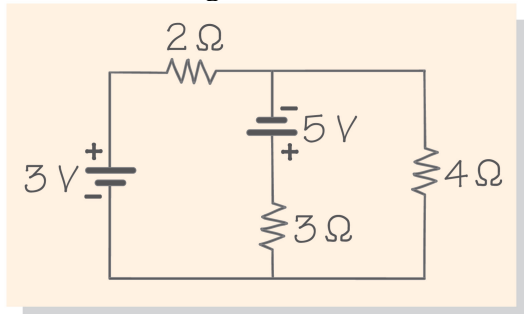
27.20. (II) Find the current that passes through the $4\text{-}\Omega$ resistor in the circuit shown in Fig. 27-31.



Copyright © 2005 Pearson Prentice Hall, Inc.

27.21. (II) Three resistors connected in parallel have resistances of $250\ \Omega$, $420\ \Omega$, and $510\ \Omega$, respectively. The total current passing through the set is $0.020\ \text{A}$. What is the potential difference across the set, and what are the currents in each of the resistors?

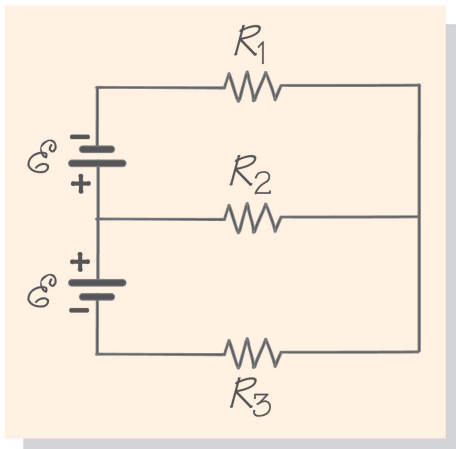27.22. (II) Can the resistors of the circuit in Fig. 27-32 be reduced to a single equivalent circuit by application of the rules for circuits with connections in parallel and in series? Solve for the currents through the three resistors.



Copyright © 2005 Pearson Prentice Hall, Inc.