

2/15 In Class: Thevenin Equivalent

Do these problems before starting Lab 4 and check your work with each other and me

You may work in groups at the lab tables or at the white board. If you work on the white board, I am happy to take pics and make them available on google drive.

14. \otimes (1e:1.8) We now attach two output terminals to the circuit from problem 13. The resulting circuit is shown in in Figure 1.40. (a) What is the voltage between the terminals G and H ? (b) What current flows from G to H ? (c) If we connect a wire from G to H , what current flows through the wire and what is the voltage between G and H ?

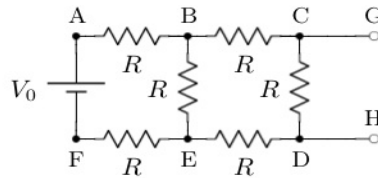


Figure 1.40: The circuit for problem 14.

15. You measure the potential difference across a $10\text{ k}\Omega$ resistor to be 10 V . What is the current flowing through the resistor?
16. (1e:1.9) Replace the circuit from problem 14 with the simpler one shown in Figure 1.41. V_{th} is a voltage source and R_{th} is a new resistance. What are the values of V_{th} and R_{th} such that you get th

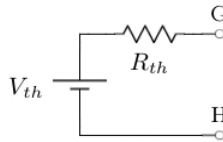


Figure 1.41: The circuit for problem 16.

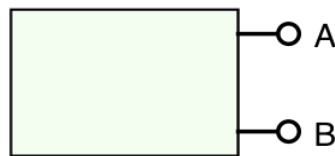


Figure 1.42: The electrical device for problem 17.

25. \otimes (1e:1.16) Determine the parameters of the Thévenin equivalent for the circuit shown in Figure 1.45.

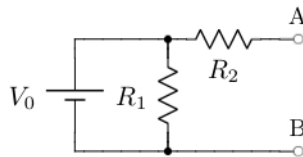


Figure 1.45: The circuit for problem 25.