

Exam 1

Physics 181, Friday Oct 6

You may use a 3"x5" card of notes, both sides. NO PHONES.

Present *clear and complete* answers.

Unjustified answers will earn no points. Any person who has taken this class should be able to understand what you did just by reading your solution. A diagram and a few words usually help. Start calculations with definitions (*e.g.* $\vec{v} \equiv \frac{d\vec{r}}{dt}$), facts (*e.g.* Newton's laws), or commonly used equations (*e.g.* constant acceleration equations).

1. **Two resistors are in series with a battery. Determine the voltage and current for each resistor.**

2. Two resistors are in parallel with a battery. Determine the voltage and current for each resistor.

3. Calculate the equivalent resistance between any two points in a resistor network.

4. Analyze a circuit using Kirchoff's rules. This means
(a) **writing the voltage and current equations**
(b) determining the current through any branch
(c) calculating the voltage across any element
(d) calculating the power for each element.

5. Describe how to measure the IV characteristic of a passive element. Provide text and a circuit diagram. What information can you get from the IV curve of a passive element?

6. What is a resistive, or ohmic, element? Describe its behavior and give an example. Equations and diagrams/graphs are always helpful.

What is an ideal voltage source? Describe its behavior and give an example. Equations and diagrams/graphs are always helpful.

7. Describe how to measure the load curve of an active element. Provide text and a circuit diagram.

What information can you get from the load curve of an active element?

What type of resistance is considered a "large load"? Explain.

8. (a) What does a voltage divider do?
(b) Derive the output of an unloaded voltage divider,

$$V_{\text{out}} = \frac{R_2}{R_1 + R_2} V_{\text{in}}$$

(c) Design a voltage divider to output a desired output voltage. You'll be given an input voltage, a load resistance, and a maximum power for the circuit. You'll have to provide resistor values, a circuit diagram, and specify the input and output terminals.

9. What is equivalent between the Thévenin equivalent circuit and the circuit it models?

10. (a) How can you measure a circuit's Thévenin equivalent voltage and resistance? In addition to text, include a circuit diagram.

(b) Analytically determine the Thévenin equivalent of a circuit consisting of resistors and voltage sources.

11. Derive the following expressions for the Thévenin equivalent voltage and resistance for a voltage divider.

$$V_{\text{Th}} = V_0 \frac{R_2}{R_2 + R_1}$$
$$R_{\text{Th}} = \frac{R_1 R_2}{R_1 + R_2}$$

where V_0 is the input voltage to the divider and the output is taken across R_2 .

12. A circuit is designed to deliver power and voltage to a load (R_L). The circuit will provide

- (a) a maximum voltage when $R_L \gg R_{\text{Th}}$
- (b) maximum power to the load when $R_L = R_{\text{Th}}$.

Derive the above results. Start with the circuit diagram for the Thévenin equivalent circuit, a Kirchoff loop, and $V = IR$. Explain your steps.

13. Measured quantities have uncertainties. Determine the uncertainty of a value calculated from measurements.

For example, $E = kq/r^2$. If $q = 2.05\text{nC} \pm 0.03\text{nC}$ and $r = 6.1 \pm 4\%$, calculate $E \pm \Delta E$

Items 1 and 4a will definitely be on the test. They're all or nothing problems; no partial credit. They're the first 3 problems of the test. You will not be allowed to use your notecard for these 3 problems.