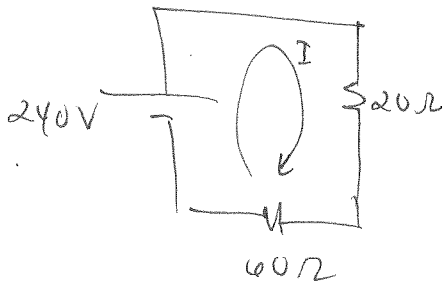


# Exam 1 - Solutions

## Part I

i.



$$+240 - I(20+60) = 0$$

$$I = \frac{240}{80} = 3A \quad \text{for both resistors}$$


$$V = IR$$

$$= (3)(20) = 60V \quad \text{for } 20\Omega \text{ resistor}$$

$$V = IR$$

$$= 3(60) = 180V \quad \text{for } 60\Omega \text{ resistor}$$

ii.

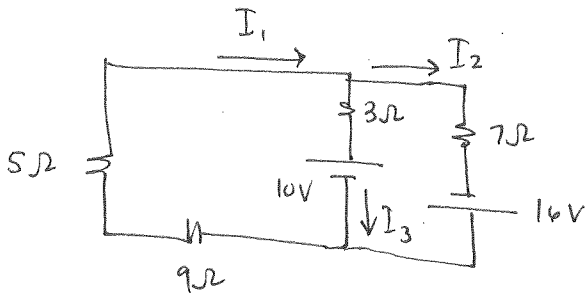

current/  
jnc rule

$$I_1 - I_2 - I_3 = 0$$

voltage/  
loop rule:

$$I_3 + I_2 - I_1 = 0$$

$$\text{left loop} \quad -5I_1 - 3I_2 - 10 - 9I_1 = 0$$

$$\text{right loop} \quad +10 + 3I_3 - 7I_2 + 16 = 0$$

$$\text{big loop} \quad -9I_1 - 5I_1 - 7I_2 + 16 = 0$$

to find  $I_1, I_2 + I_3$

choose any 2 loop equations


and 1 jnc. equation.

(3 equations for 3 unknowns)

# Exam 1: Solutions, part 2

$$1. R_{AB} = \left[ \frac{1}{40} + \frac{1}{30+50} \right]^{-1} = \left[ \frac{1}{40} + \frac{1}{80} \right]^{-1} = \frac{80}{3}$$

2.

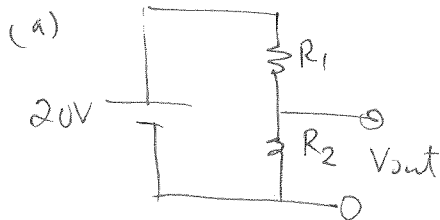

$$\text{hence, } V_{out} = 20V \cdot \frac{R_2}{R_1 + R_2}$$

So  $R_2$  needs to be  $\frac{1}{4}$  of total Resistance,

$$\text{or } 3R_2 = R_1$$

$$R_2 = \frac{R_1}{3}$$

Choose  $R_2 = 250\Omega$   
 $R_1 = 750\Omega$

- These choices satisfy  $R_L \gg R_2$  (its 100x), and its more specific requirement of  $R_L \gg R_{TH}$  (here  $R_{TH} = R_1 \parallel R_2$ )
- We also don't choose v. low  $R$ 's, since these  $R$ 's will dissipate power.

(b) No current flows through the output,

but current does flow through  $R_1 + R_2$  at all times.

The divider itself dissipates power, even when there's no load.

$$3/ \quad E = E_0 + \frac{1}{2} kx^2$$

$$dE = dE_0 + \frac{1}{2} k(2x) dx$$

$$\Delta E = \Delta E_0 + kx \Delta x$$


$$\text{here, } \Delta E_0 = 3$$

$$\Delta x = 4 \times (0.1) = 0.4$$

$$\Delta E = 3 + (10)(4)(0.4)$$

$$\Delta E = 19 \text{ J}$$


4/

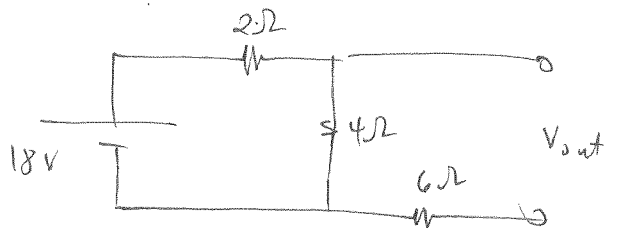

here,  $V_{TH} = V_{out}$  when there's no load

In this case, there's no current through the  $6\Omega$  resistor +

$$V_{out} = V_{4\Omega}$$

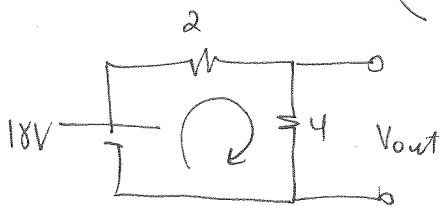


$$18V - I(2+4) = 0$$

$I = 3 \text{ A}$ , the current through  $2\Omega + 4\Omega$  resistors.

$$V_{4\Omega} = IR$$


$$= 3(4) = 12 \text{ V}$$

5/

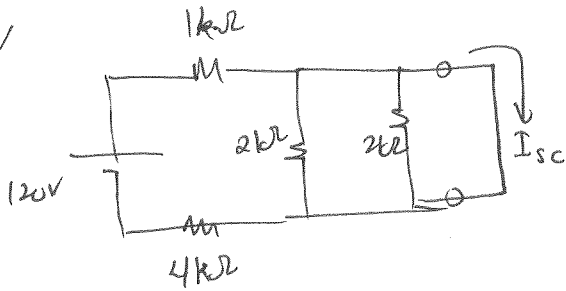

$$R_{TH} = \frac{V_{TH}}{I_{sc}}$$

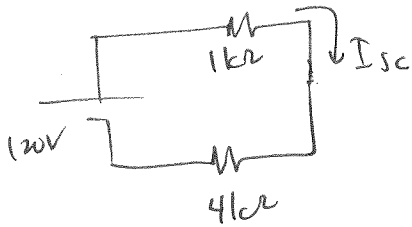
In this case, the short circuit means the 2kΩ resistors don't play a part in the circuit



$$I_{sc} = \frac{12V}{5k\Omega} = 24mA$$

$$R_{TH} = \frac{20V}{24mA} = 833\Omega$$

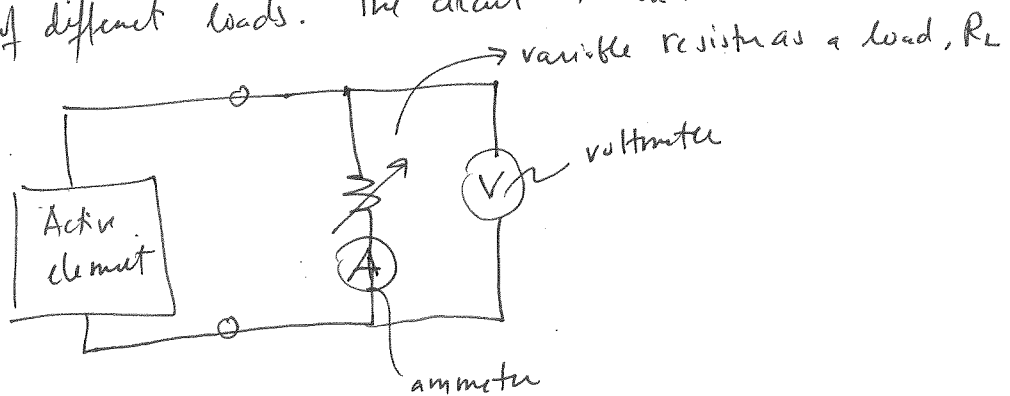
6/ The load curve of an active element is experimentally determined by measuring the voltage & current supplied by the element to a set of different loads. The circuit to use:




measure V, I for different  $R_L$ 's

7/ (a) Its load curve.. That is, the voltage (and power) supplied to an output.

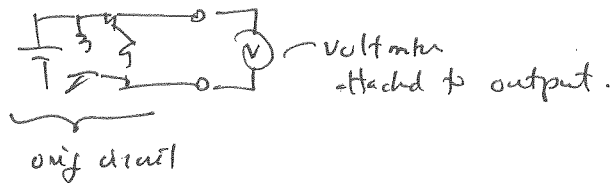(b) The Thevenin voltage is the open circuit voltage



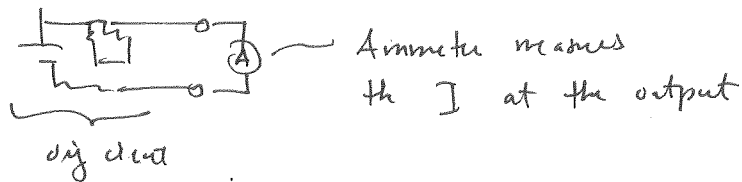The Thevenin resistance is  $\frac{V_{TH}}{I_{sc}}$ , where  $I_{sc}$  is the short circuit current.



8/

ideal voltage source

any Thevenin circuit; for example a v-divider

a resistor

a diode