

Exam 2 - solution

1/ $G = 0.25 e^{+j\pi/4}$ this is of the form $G = |G| e^{j\phi}$


so $|G| = 0.25$

or $V_{out} = 0.25 V_{in}$

$\Delta\phi = \frac{\pi}{4} \rightarrow \frac{\Delta\phi}{2\pi} = \frac{\Delta t}{T}$

$\Delta t = \frac{\Delta\phi}{2\pi} T = \frac{\pi}{4} \frac{(20\text{ms})}{2\pi}$

$= \frac{20}{8} = 2.5\text{ms}$

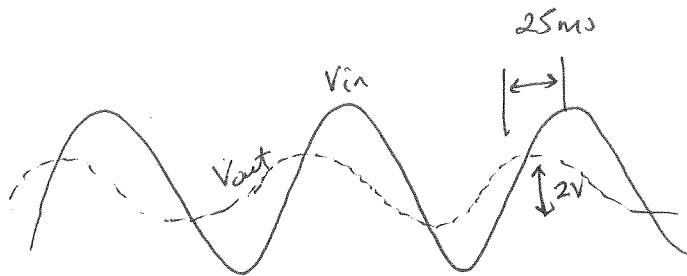

2/ (a) $G = \frac{\left(\frac{1}{Z_L} + \frac{1}{Z_R}\right)^{-1}}{Z_{C1} + Z_{C2} + \left(\frac{1}{Z_L} + \frac{1}{Z_R}\right)^{-1}} = \frac{\left(\frac{1}{j\omega L} + \frac{1}{R}\right)^{-1}}{\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} + \left(\frac{1}{j\omega L} + \frac{1}{R}\right)^{-1}}$

(b) $Z_{in} = Z_{eq} = Z_{C1} + Z_{C2} + \left(\frac{1}{Z_L} + \frac{1}{Z_R}\right)^{-1}$
 $= \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} + \left(\frac{1}{j\omega L} + \frac{1}{R}\right)^{-1}$

(c) $Z_{out} = Z_{TH} = \frac{Z_1 Z_2}{Z_1 + Z_2}$ if it "looks like" a v-divider
 $= \frac{\left(\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2}\right) \left(\frac{1}{j\omega L} + \frac{1}{R}\right)^{-1}}{\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} + \left(\frac{1}{j\omega L} + \frac{1}{R}\right)^{-1}}$

$$3/ \quad (a) \quad |G| = \sqrt{G^* G} = \left[\frac{R}{(R+R_L) - j(\omega L)} \cdot \frac{R}{(R+R_L) + j(\omega L)} \right]^{1/2}$$

$$= \left[\frac{R^2}{(R+R_L)^2 + (\omega L)^2} \right]^{1/2}$$

$$(b) \quad G = \frac{R}{(R+R_L) + j\omega L} \cdot \frac{(R+R_L) - j\omega L}{R+R_L - j\omega L} = \frac{R(R+R_L) - jR\omega L}{(R+R_L)^2 + (\omega L)^2}$$

$$\tan \theta = \frac{\text{Im part}}{\text{Re part}} \rightarrow \theta = \arctan \left(\frac{-\omega R L}{R(R+R_L)} \right)$$

$$\theta = \arctan \left(\frac{-\omega L}{R+R_L} \right)$$

$$(c) \quad \lim_{\omega \rightarrow 0} |G(\omega)| = \left[\frac{R^2}{(R+R_L)^2 + 0} \right]^{1/2} = \frac{R}{R+R_L}$$

$$\lim_{\omega \rightarrow \infty} |G(\omega)| = \left[\frac{R^2}{(R+R_L)^2 + \infty} \right]^{1/2} = 0$$


(d) This is a lp filter

$G \rightarrow 0$ in high frequencies

but it's not a good lp filter since $G < 1$ at $\omega \rightarrow 0$

4/ (a) This is a high pass filter $G \rightarrow 1$ at high ω
 $G \rightarrow 0$ at low ω

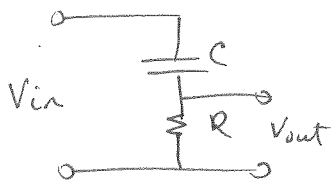(b) A typical hp filter is an RC circuit. (There are other hp filters.)



Here, $|G| = \left[\frac{1}{1 + \left(\frac{\omega_{RC}}{\omega}\right)^2} \right]^{1/2}$ when $\omega = \omega_{RC}$, $|G| = \frac{1}{\sqrt{2}} = 0.707$


So 200 Hz is f_{RC}

$$2\pi f_{RC} = \omega_{RC} = \frac{1}{RC}$$

$$RC = \frac{1}{2\pi(200\text{ Hz})}$$

for $R = 1\text{ k}\Omega$ $C = 0.8\ \mu\text{F}$
 (can choose any RC combination... but RC choice will determine $Z_{in} + Z_{out}$ for this filter.)

5/

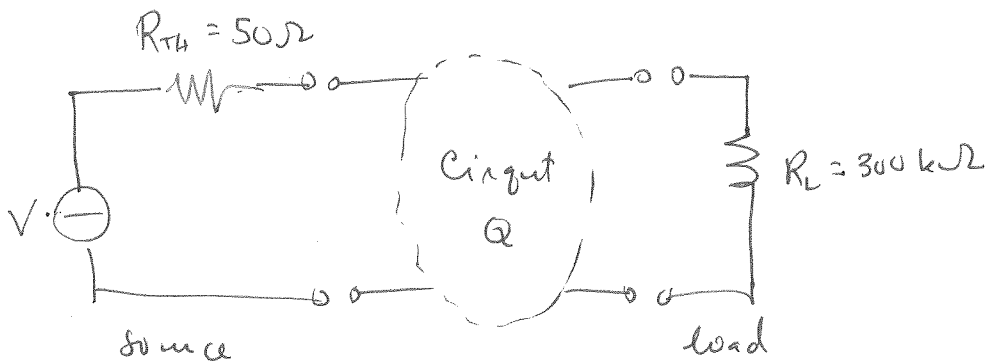

(a) Z_{in} of circuit Q $\gg Z_{TH}$ of source circuit.

$$5\text{ k}\Omega \gg 50\Omega$$

so Z_{in} is $100 \times Z_{out}$.

Z_{out} of circuit Q $\ll Z_L$ of load

$$3\text{ k}\Omega \ll 300\text{ k}\Omega$$

that's $100 \times$ smaller than Z_L

(b) They're "good" because it will allow for

- using $G(\omega)$ expressions for each stage

- the V-signal transfer to each stage is maximized ($V \approx V_{TH}$ of each stage)

- therefore, largest signal transfer to output

If this isn't followed, will have signal attenuation.

i.e. it will be smaller.

6/ The impedance of a component defines the proportionality between the voltage + current of the component,

$$V = IZ \quad (1)$$

For a capacitor, its capacitance is $C = \frac{Q}{V}$. (2)

Rearrange Eqn (2) to be of the form of eqn (1).

We know that $\frac{dq}{dt} = i$

$$q = \int i dt$$

So (2) becomes

$$V(t) = \frac{Q(t)}{C} = \frac{\int i dt}{C}$$

Now let $i(t) = i_0 e^{j\omega t}$

$$V(t) = \frac{1}{C} \int i_0 e^{j\omega t} dt$$


$$= \frac{1}{j\omega C} i_0 e^{j\omega t}$$

$$V(t) = \frac{1}{j\omega C} i(t)$$

Compare to Eqn (1)

therefore $Z_C = \frac{1}{j\omega C}$

7/

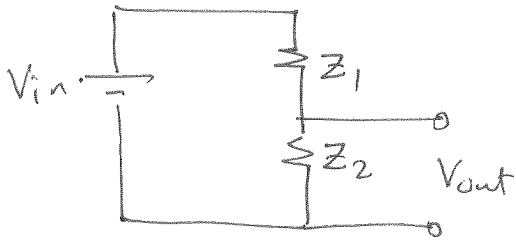

$V_{TH} = V_{out}$ of unloaded divider. Therefore, $V_{TH} = V_{out} = V_{Z_2}$

K. loop: $+V_{in} - IZ_1 - IZ_2 = 0$


$$I = \frac{V_{in}}{Z_1 + Z_2}$$

Ohm's law: $V_{Z_2} = IZ_2 = \frac{V_{in} Z_2}{Z_1 + Z_2}$

therefore $V_{TH} = \frac{Z_2}{Z_1 + Z_2} V_{in}$

now $Z_{TH} = \frac{V_{TH}}{I_{sc}}$

where

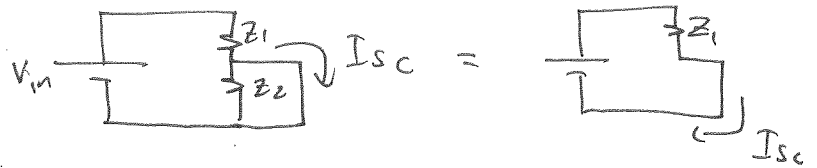

so $I_{sc} = \frac{V_{in}}{Z_1}$

$$Z_{TH} = \frac{Z_2}{Z_1 + Z_2} V_{in} \frac{Z_1}{V_{in}}$$

$$Z_{TH} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

- 8/ • linear scales are useful if your dataset spans only 1 or 2 orders of magnitude.

For example, $(0.1, 0.2 \dots 1 \dots 10.1)$
 or $(1010, 1020 \dots 2050 \dots 5405)$

} we should be able to see 0.1 + 10.1 both easily
 or 1010 + 5405 easily

- log scales are useful if your dataset spans several orders of magnitude

For example, $(0.1, 1, 10, 100, 1000, 10,000)$

Plotting such a dataset on a linear scale, we'd lose any sense on what's going on at the 0.1 + 1 region if our range = $0 \rightarrow 10^4$.

- In addition, log scales are useful for determining exponential or power-dependencies.

For example, if $g = h^3$ or $\frac{V}{V_0} = e^{-t/RC}$

$\underbrace{(\ln g)}_{\text{on y-axis}} = 3 \underbrace{(\ln h)}_{\text{on x-axis}}$
 will give a line w/ slope of 3

$\underbrace{\ln\left(\frac{V}{V_0}\right)}_{\text{plot on y}} = \underbrace{-\frac{t}{RC}}_{\text{plot t on x}}$
 will give a line w/ slope of $-\frac{1}{RC}$

9/ RLC filter has 3 possible outputs: V_C , V_R , V_L

Two of these (V_C , V_L) can have gain > 1 at the resonant frequency.

RC bandpass only has one possible output, with $g < 1$.

• RLC will have a phase shifted output at ω_{RC}

RC bandpass isn't phase shifted at ω_{RC}